

29. The two voltage sources have been in the circuit of figure P8.29 for a long time. Compute $i_L(t)$ for $t \geq 0$. Plot your answer using MATLAB or equivalent for $0 \leq t \leq 5\tau$.

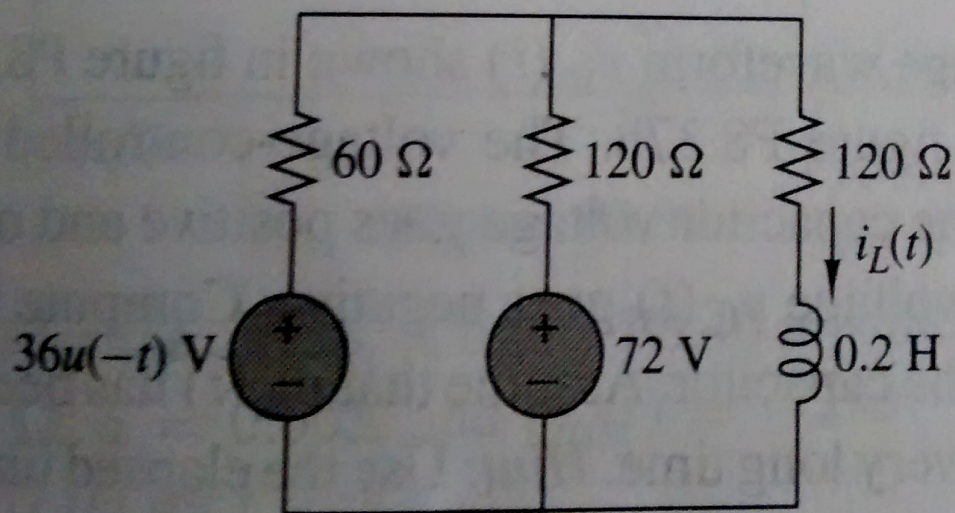


Figure P8.29

30. The two voltage sources have been in the circuit of figure P8.30 for a long time. Compute $v_C(t)$ for $t \geq 0$. Plot your answer using MATLAB or equivalent for $0 \leq t \leq 5\tau$.

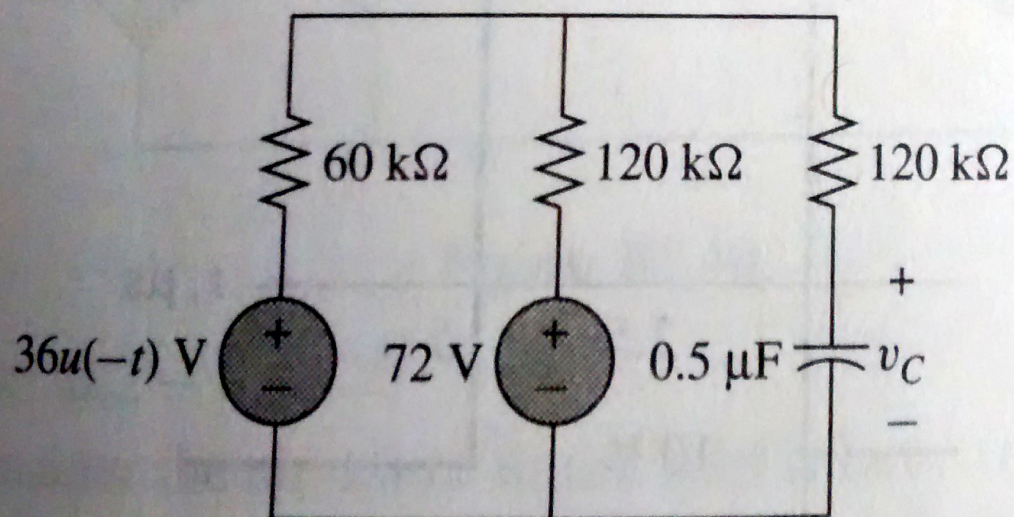


Figure P8.30

33. Consider the circuit of figure P8.33 in which the indicated source excitations are valid for all time.

- (a) Compute the response $i_L(t)$ for $t \geq 0$. Plot for $0 \leq t \leq 5\tau$, where τ is the circuit time constant.
- (b) Find the inductor voltage $v_L(t)$ for $t > 0$ directly using equation 8.23.
- (c) What are the new responses if the value of each source is doubled?

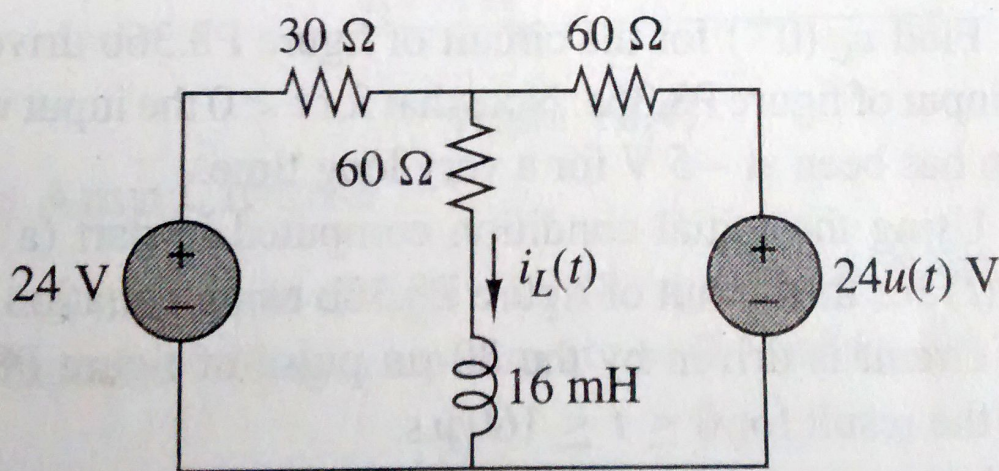


Figure P8.33

35. Consider the circuit of figure P8.35 in which the switch opens at $t = 0.5$ s.

- Find $v_C(0^-)$.
- Find $v_C(0^+)$. Justify your answer.
- Compute the time constant τ_1 valid for $0 \leq t < 0.5$ s.
- Construct an expression for $v_C(t)$ valid for $0 \leq t < 0.5$ s.
- Compute $v_C(0.5^+)$.
- Compute the time constant τ_2 valid for $t \geq 0.5$ s.
- Find an expression for $v_C(t)$ valid for $t \geq 0.5$ s.
- Sketch the waveform for $0 \leq t \leq 2.4$ s using MATLAB.

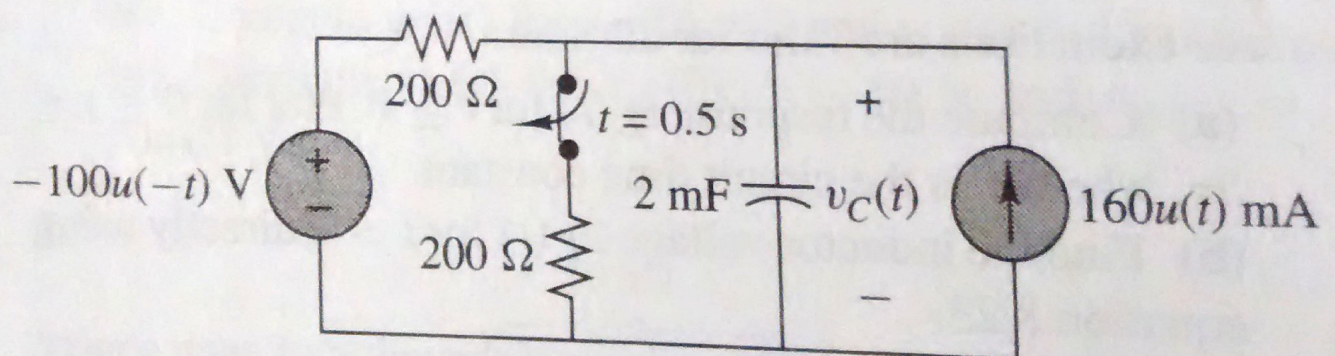


Figure P8.35

12. For the circuit of figure P9.12, determine L so that the frequency of the sinusoidal response, for $t > 0$, is 5000 Hz. (Be careful about units!) Now find $v_C(0^-)$, $v_C(0^+)$, $i_C(0^-)$, $i_C(0^+)$, and $v_C(t)$ for $t > 0$.

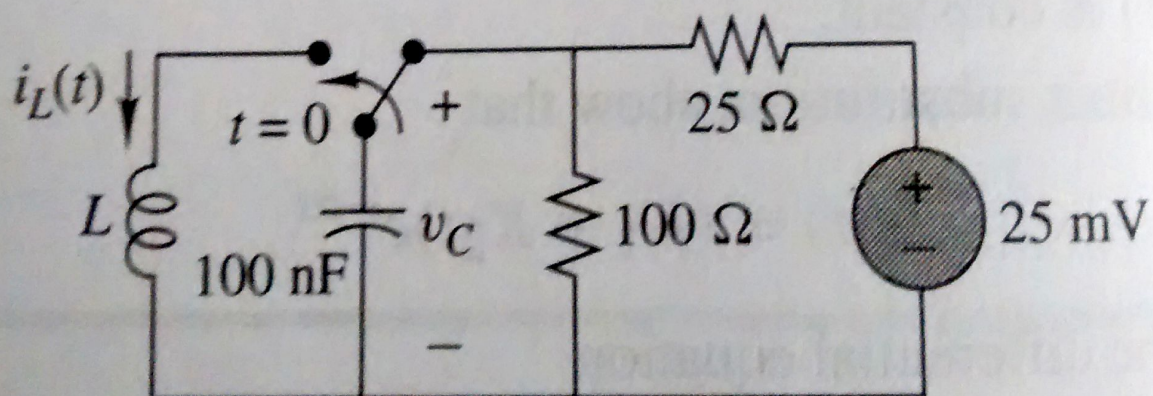


Figure P9.12

18. In figure P9.18, the switch S has been at position A for a long time and is moved to position B at $t = 0$.

(a) Find $v_C(t)$ for $t > 0$.

(b) Find $i_L(0^+)$, $i_L(\infty)$, and $i_L(t)$ for $t > 0$.

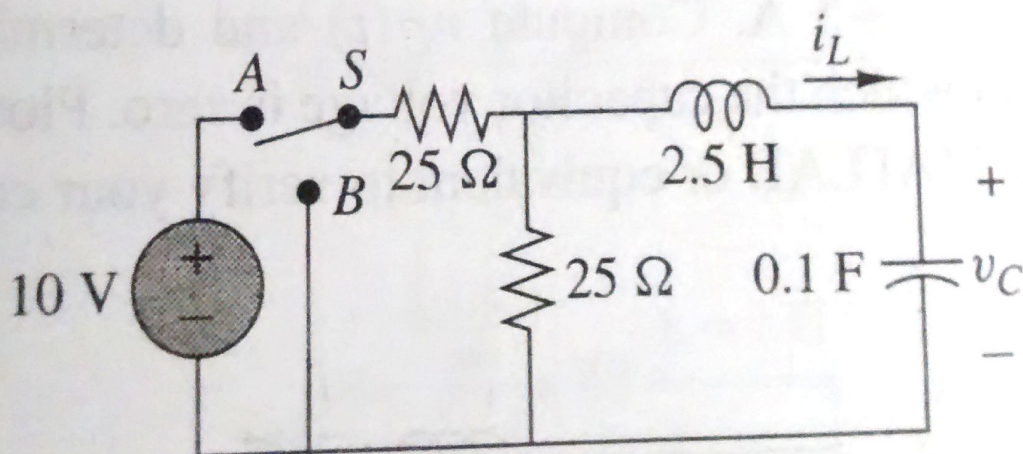


Figure P9.18